



Faculty of Engineering and Technology
Department of Electrical and Computer Engineering

ENCS3310

Advanced Digital Design

Course Project

Prepared by:

Name: Ali Shaikh Qasem ID: 1212171

Instructor: Dr. Abdallatif Abuissa.

Section: 1.

first-semester

2023/2024

Abstract

This project aims to build a simple model of a microprocessor. specifically, to build an ALU and a simple register file, then connect them together and manage the synchronization between them. In addition, to simulate a simple machine code program and test the design.

Contents

Theory	4
Arithmetic Logic Unit (ALU).....	4
Register file	4
Microprocessor.....	4
Procedure & Discussion	5
ALU design	5
Register file design	6
Microprocessor design.....	7
Microprocessor testing	8
Conclusion	11
Appendix 1	12

Table of Figures

FIGURE 1: ALU SCHEMATIC	4
FIGURE 2: REGISTER FILE SCHEMATIC	4
FIGURE 3: MICROPROCESSOR SCHEMATIC	4
FIGURE 4: VERILOG CODE FOR THE ALU.....	5
FIGURE 5: REGISTER FILE CODE	6
FIGURE 6: MICROPROCESSOR CODE	7
FIGURE 7: MICROPROCESSOR TEST PART1.....	9
FIGURE 8: MICROPROCESSOR TEST PART2.....	9
FIGURE 9: MICROPROCESSOR TEST RESULTS.....	10
FIGURE 10: INSTRUCTION 1 SIMULATION.....	12
FIGURE 11: INSTRUCTION 3 SIMULATION.....	12
FIGURE 12: INSTRUCTION 4 SIMULATION.....	12
FIGURE 13: INSTRUCTION 5 SIMULATION.....	13
FIGURE 14: INSTRUCTION 6 SIMULATION.....	13
FIGURE 15: INSTRUCTION 7 SIMULATION	13
FIGURE 16: INSTRUCTION 8 SIMULATION.....	13
FIGURE 17: INSTRUCTION 9 SIMULATION.....	14
FIGURE 18: INSTRUCTION 10 SIMULATION.....	14
FIGURE 19: INSTRUCTION 11 SIMULATION.....	14

Theory

Arithmetic Logic Unit (ALU)

Alu is a combinational circuit that performs arithmetic operations like addition and subtraction, and also a logical bitwise-operations like bitwise and. It has two inputs represents the operands and a selection input that determines the operation to perform and a result output.

 


Figure 1: ALU schematic

Register file

Register file is a very small amount of memory inside the processor. It's a clocked circuit used to hold the operands that the processor is currently working on. It has three addresses inputs, two of them represents the address of the required values, and the other represents the address of which the input value will be stored.

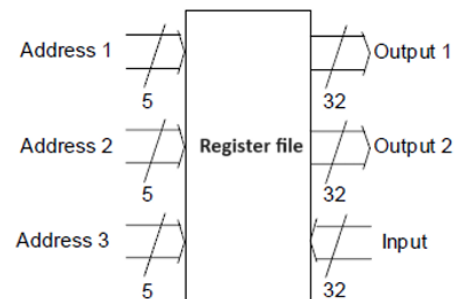


Figure 2: Register file schematic

Microprocessor

Microprocessor is a simple CPU that runs a program by executing the instructions. It consists of the ALU and register file, it uses the register file to fetch the operands and store the results, and it uses the ALU to perform the operation on the operands.

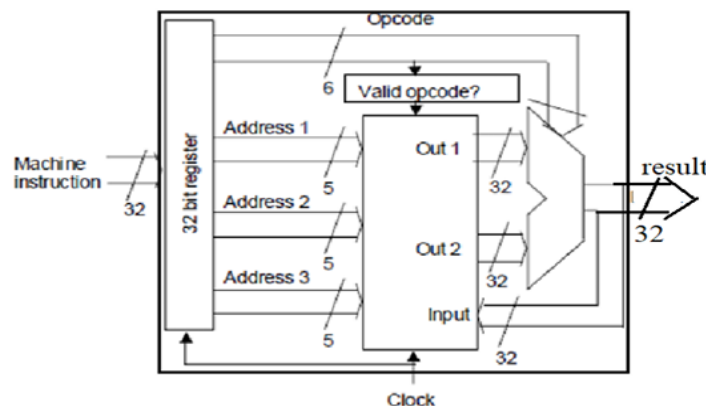


Figure 3: Microprocessor schematic

Procedure & Discussion

ALU design

- The Verilog description of the ALU:

```
module alu (opcode, a, b, result );
    input [5:0] opcode;
    input signed [31:0] a, b;
    output reg signed [31:0] result;

    always @(*)
    begin
        case (opcode)
            6'b000110 : result = a + b; //a+b
            6'b001000 : result = a - b; //a-b
            6'b001010 : begin //|a|
                if(a >= 0)
                    result = a;
                else
                    result = -a;
                end
            6'b001100 : result = -a; //-a
            6'b001110 : begin //max(a,b)
                if(a > b)
                    result = a;
                else
                    result = b;
                end
            6'b001111 : result = ~a; //not a
            6'b000010 : result = a | b; // a or b
            6'b000011 : result = a & b; // a and b
            6'b001001 : result = a ^ b; // a xor b
            default: result = 32'bx;
        endcase
    end
endmodule
```

Figure 4: Verilog code for the ALU

- As seen above, we have used the behavioral modeling. The operation is determined using case statement based on the values of opcodes that are related to my id.
- Notice that We have used a signed numbers representation for the operands and results, this is to avoid wrong results especially when dealing with negative numbers and results.
- It's also noticed that in the case the opcode is not valid, the result is assigned to a don't care values.

Register file design

- The Verilog description of the register file:

```
79 module reg_file (clk, valid_opcode, addr1, addr2, addr3, in , out1, out2);
80
81     //defining inputs and outputs
82     input clk;
83     input valid_opcode;
84     input [4:0] addr1, addr2, addr3;
85     input [31:0] in;
86     output reg [31:0] out1, out2;
87     //defining the register file slots
88     reg [31:0] reg_slots [0:31];
89
90     //initializing the values in the register file
91     initial
92     begin
93         reg_slots [0] = 32'h0; reg_slots [1] = 32'h3ABA; reg_slots [2] = 32'h2296; reg_slots [3] = 32'hAA;
94         reg_slots [4] = 32'h1C3A; reg_slots [5] = 32'h1180; reg_slots [6] = 32'h22E0; reg_slots [7] = 32'h1C86;
95         reg_slots [8] = 32'h22DA; reg_slots [9] = 32'h414; reg_slots [10] = 32'h1A32; reg_slots [11] = 32'h102;
96         reg_slots [12] = 32'h1CBA; reg_slots [13] = 32'hCDE; reg_slots [14] = 32'h3994; reg_slots [15] = 32'h1984;
97         reg_slots [16] = 32'h28C4; reg_slots [17] = 32'h2E7C; reg_slots [18] = 32'h3966; reg_slots [19] = 32'h227E;
98         reg_slots [20] = 32'h2208; reg_slots [21] = 32'h1B4; reg_slots [22] = 32'h237C; reg_slots [23] = 32'h360E;
99         reg_slots [24] = 32'h2722; reg_slots [25] = 32'h580; reg_slots [26] = 32'h16B6; reg_slots [27] = 32'h29E;
100        reg_slots [28] = 32'h2280; reg_slots [29] = 32'h3B52; reg_slots [30] = 32'h11A0; reg_slots [31] = 32'h0;
101    end
102
103    always @ (posedge clk)
104    begin
105        if(valid_opcode)
106        begin
107            out1 <= reg_slots [addr1];
108            out2 <= reg_slots [addr2];
109            reg_slots [addr3] <= in;
110        end
111    end
112 endmodule
```

Figure 5: register file code

From the code shown above, we notice the following points:

- The initial values of the register slots are set at the initial block based on the values related to my id.
- An input called “valid opcode” is added to the circuit to work as an enable, when the “valid opcode” bit is high, the register works normally. but when it goes to 0, the register doesn’t work. This ensures that the register avoids undesired (garbage) input values.
- The register file is connected to the clock with a positive edge, this is to avoid over-writing the register values especially when the input and output addresses are the same, and also to synchronize the circuit with the whole system.
- The statements inside the always block are designed in a way that organizes the behavior of the register, we notice that the values of the two outputs (out1 and out2) is brought firstly, and then the input value is stored in the slot addressed by the third address(addr3), we also notice that we have used the non-blocking assignment, thus, in the case the input and output addresses are the same, the value of the output will be fetched before the new value is stored.

Microprocessor design

- The Verilog description of the microprocessor:

```
145 module mp_top (clk, instruction , result );
146
147     input clk;
148     input [31:0] instruction;
149     output signed [31:0] result;
150     wire valid_opcode_result;
151     wire [31:0] out1,out2;
152
153     //defining the registers that hold the instruction and the opcode
154     reg [31:0] reg_32_out;
155     reg [5:0] opcode;
156
157     //clocking the instruction register and opcode, this is to ensure the opcode reaches the alu with the register values.
158     always @(posedge clk)
159     begin
160         reg_32_out <= instruction;
161         opcode <= reg_32_out [5:0];
162     end
163
164     // instantiate the required modules
165     valid_opcode v1 ( reg_32_out [5:0], valid_opcode_result);
166     reg_file rg1 (clk, valid_opcode_result, reg_32_out [10:6] , reg_32_out [15:11], reg_32_out [20:16], result , out1, out2);
167     alu al (opcode, out1, out2, result );
168
169     task valid_opcode ; // defining a task to check if the provided opcode is valid or not
170     input opcode;
171     output reg valid;
172
173     //checking if the opcode is valid based on my id corresponding opcodes
174     if(opcode==6 || opcode== 8 ||opcode==10||opcode==12 || opcode==14 || opcode==11 || opcode==13 || opcode==15 || opcode==2 || opcode==3 || opcode== 9)
175         valid = 1;
176     else
177         valid = 0;
178     endtask
179
180 endmodule
```

Figure 6: microprocessor code

- As seen above, the microprocessor is designed using structural modeling, so that it's possible to instantiate the ALU and register files implemented previously.
- It's noticed that we have also defined a 32-bit register called "reg_32_out" to store the instruction, so that the instruction will be available in the microprocessor after a clock cycle.
- We have also defined a 6-bit register to store the opcode which is the first 6 bits of the instruction (instruction[5:0]) and we connected it to the clock, this is to apply a one cycle delay before the opcode reaches the ALU, notice that we have used the non-blocking assignment inside always block, so that the target opcode value will reach the ALU exactly after two cycles at the same moment the register value arrives.
- The overall design shows that the instruction will be performed in a total of two clock cycles, one for fetching the instruction and the other one for fetching the operands from the register file, while the ALU will produce the result at the same moment it's inputs changes. Additionally, it's crucial to notice that storing the result in the destination register will also spend a clock cycle, so we need to provide an additional cycle in the test

to ensure the result has been stored or we use a no opcode instruction that instructs the CPU to do nothing while the value is stored.

- We have also added a task called “valid opcode” to test whether the provided opcode in the instruction is valid or not, the validity here depends on the opcodes related to my id. If the opcode is not valid then, the task will return 0 , thus, the register file will not work, otherwise, everything works normally.

Microprocessor testing

- In this part, we are going to create a program consists of multiple instructions, and execute them using the designed microprocessor.
- The table below describes the created instructions:

Instruction	opcode	Src1	Src2	Destination	Description
0X142006	6	R[0]	R[4]	R[20]	Add R[0] to R[4] and store the result in R[20].
0X1508C8	8	R[3]	R[1]	R[21]	Subtract R[3] - R[1] and store the result in R[21].
0X16054A	10	R[21]	x	R[22]	Get the absolute value of R[21] and store it in R[22].
0X17014C	12	R[5]	x	R[23]	Get the value of -R[5] and store it in R[23].
0X18398E	14	R[6]	R[7]	R[24]	Get the maximum value of R[6] and R[7] and store it in R[24].
0X192B4B	11	R[13]	R[5]	R[25]	Get the minimum value of R[13] and R[5] and store it in R[25].
0X1A7B8D	13	R[14]	R[15]	R[26]	Get the average value of R[14] and R[15] and store it in R[26]
0X1B044F	15	R[17]	x	R[27]	Get the value of not R[17] and store it in R[27]
0X281842	2	R[1]	R[3]	R[28]	Get the bitwise or of R[1] and R[3] and store it in R[28].
0X1D4B03	3	R[12]	R[9]	R[29]	Get the bitwise and of R[12] and R[9] and store it in R[29].
0X1E9089	9	R[2]	R[18]	R[30]	Get the bitwise xor of R[2] and R[18] and store it in R[30].

- The test bench code is shown below:

```

184 module mp_test ();
185
186     reg [31:0] instruction;
187     reg clk;
188     wire signed [31:0] result;
189     // defining the array of instructions, it includes 11 instructions, that means an instruction for every opcode.
190     reg [31:0] instructions [0:10] = '{32'h00142006, 32'h001508C8, 32'h0016054A, 32'h0017014C, 32'h0018398E, 32'h00192B4B,
191     32'h001A7B8D, 32'h001B044F, 32'h00281842, 32'h001D4B03, 32'h001E9089};
192     // defining the array of expected values for the written instructions
193     reg [31:0] expected_values [0:10] = '{32'h1C3A, 32'hFFFC5F0, 32'h3A10, 32'hFFFFEE80, 32'h22E0, 32'h0CDE, 32'h298C, 32'hFFFD183,
194     32'h3ABA, 32'h0410, 32'h1BF0};
195
196     int flag = 0; // 0 means pass and 1 means fail.
197
198     mp_top m1 (clk, instruction , result );
199
200     initial
201     begin
202         $display("      Instruction      Result      status ");
203         $display("      -----");
204
205         clk = 0;
206         instruction = instructions[0];
207         #20ns // to execute the first instruction
208         if(result == expected_values[0])
209             $display("      0x%0h      %0d      pass ", instruction, result);
210         else
211             begin
212                 $display("      0x%0h      %0d      fail ", instruction, result);
213                 flag = 1;
214             end
215     end
216

```

Figure 7: microprocessor test part1

```

216
217     for(int i=1 ; i<=10 ; i=i+1)
218     begin
219         instruction = instructions[i];
220         #35ns; // 3 cycles, two for executing the instruction and one for storing the result in the destination
221         if(result == expected_values[i])
222             $display("      0x%0h      %0d      pass ", instruction, result);
223         else
224             begin
225                 $display("      0x%0h      %0d      fail ", instruction, result);
226                 flag = 1;
227             end
228     end
229     // determine if the test fails or passes
230     if(flag == 1)
231         $display("The test fails");
232     else
233         $display("The test passes");
234
235     end
236
237
238     always #5ns
239     clk = ~clk;
240
241 endmodule
242
243
244

```

Figure 8: microprocessor test part2

- As shown above, both the instructions and the expected values are stored in an array of registers, to be compared with the calculated values.
- We have defined a flag variable called “flag” to check whether the test passes or fails, as long as the flag equals 0 the test passes, but once it reaches 1 the test fails.
- At the beginning of the initial block, the clock is initialized to zero and the instruction takes the value of the first instruction in the program. The clock cycle is set to 10ns also.

Notice that we have a 20ns delay after the first instruction, first 5 seconds for waiting the first positive edge to occur, and the remaining 15ns to execute the instruction.

- We have defined a loop to execute the remaining 10 instructions. Notice that each instruction must wait 35ns which is 3 cycles to ensure the instruction completes the execution and the result is stored in the destination register before going to the next instruction.
- The console result of the test bench is shown below:

```

◦ run 700 ns
◦ # KERNEL:      Instruction      Result      status
◦ # KERNEL:      -----
◦ # KERNEL:      0x142006          7226        pass
◦ # KERNEL:      0x1508c8          -14864       pass
◦ # KERNEL:      0x16054a          14864        pass
◦ # KERNEL:      0x17014c          -4480        pass
◦ # KERNEL:      0x18398e          8928         pass
◦ # KERNEL:      0x192b4b          3294         pass
◦ # KERNEL:      0x1a7b8d          10636        pass
◦ # KERNEL:      0x1b044f          -11901       pass
◦ # KERNEL:      0x281842          15034        pass
◦ # KERNEL:      0x1d4b03          1040         pass
◦ # KERNEL:      0x1e9089          7152         pass
◦ # KERNEL: The test passes
◦ # KERNEL: stopped at time: 700 ns
◦

```

Figure 9: microprocessor test results

- As results above indicates that all calculated results are equivalent to expected values, thus, the test passes.
- Notice that the third instruction gets the absolute value of R[21] which has been modified in the second instruction, the test shows that it actually gets the absolute value of the previous result which is (-14864), so that we ensure the process of storing results in the register file has been done successfully.

Note: see appendix 1 to view the simulation results for each instruction.

Conclusion

In this project, we have used the knowledge of digital systems design and hardware description language to create a simple meaningful microprocessor system. The design process has started by implementing the individual parts such as ALU and register file based on their behavior, then, the different modules has been connected together forming a perfect microprocessor system. One of the main issues of the design process was the challenge of synchronizing the individual parts, and organizing their timing based on a single clock. Actually, we have realized that the timing and synchronization considerations have a crucial effect on the circuit behavior, so the design procedure must deal with them seriously. Since the design verification is one of the most important steps in the design procedure, we have created a complete test bench represents a simple program that performs every opcode operation. From the test results and simulation, we can conclude that our design works fine.

Appendix 1

 


Figure 10: instruction 1 simulation

 


Figure 11: instruction 2 simulation

 


Figure 11: instruction 3 simulation

 


Figure 12: instruction 4 simulation

 


Figure 13: instruction 5 simulation

 


Figure 14: instruction 6 simulation

 


Figure 15: instruction 7 simulation

 


Figure 16: instruction 8 simulation

 


Figure 17: instruction 9 simulation

 


Figure 18: instruction 10 simulation

 


Figure 19: instruction 11 simulation